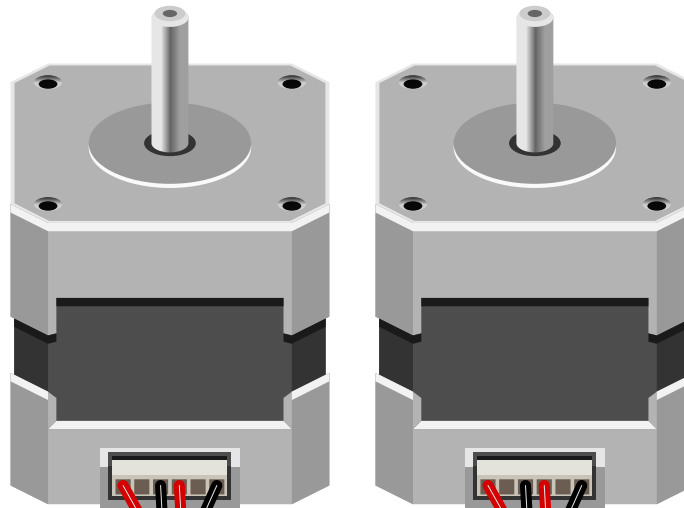
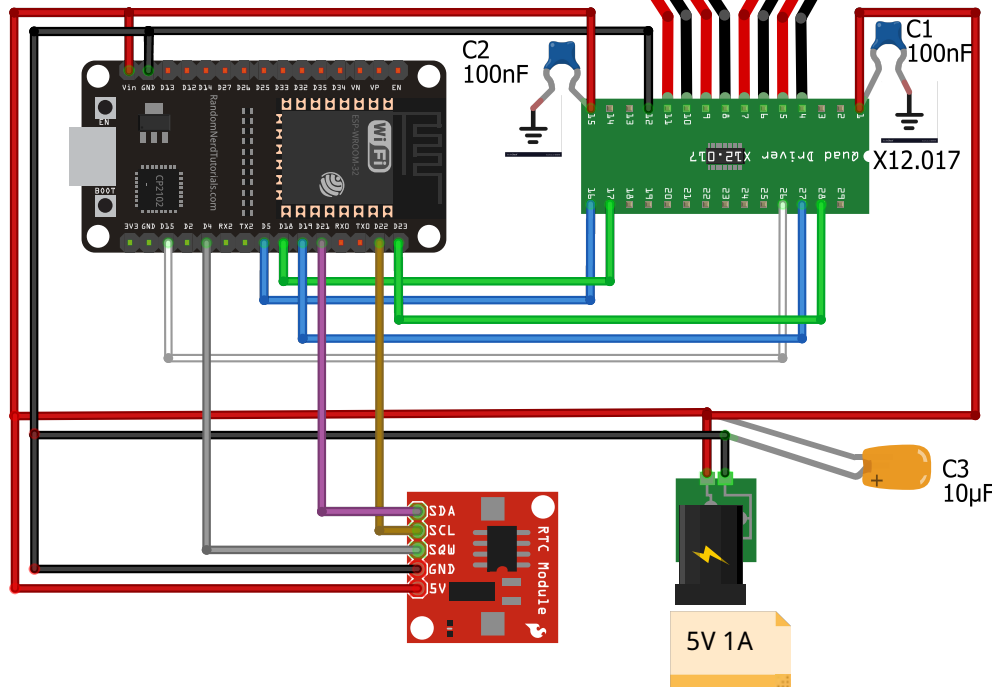


Two stepper motors compined = X40 stepper motor



Note that which motor wires goes to which motor driver outputs is important

Breadboard hardware design for SingleClock



22 uF if 4 motors, as recommended by X12.017 datasheet